

Machine Structures 2 exam solution

Exercise 1 : (4 points)

1. The purpose of studying Digital Electronics in a Computer Science course is to understand the fundamental hardware principles and building blocks upon which computers and their components are designed and operate. (1 point)

2. A Multiplexer selects/chooses one of several input signals and forwards the selected input to a single output line. (1 point)

3. The input 1011 has three '1's, which is an odd number. Therefore, the Parity Controller would output 1. (1 point)

4. After the first rising edge on a JK-FlipFlop with (J, K) = (1,0) :

$$Q = 1$$

$$\overline{Q} = 0 \text{ (0.5 point)}$$

After the second rising edge with (J, K) = (1,1) :

$$Q = 0$$

$$\overline{Q} = 1 \text{ (0.5 point)}$$

Exercise 2 : (5 points + 1 bonus)

1. 5-steps method :

Step 2 : Truth Table (1.5 point)

E3	E2	E1	E0	P1	P0	V
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1

1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

Step 3 : Conjunctive Canonical Functions (0.75 point)

$$P1(E3,E2,E1,E0) = (E3+E2+E1+E0) \cdot (E3+E2+E1+\overline{E0}) \cdot (E3+E2+\overline{E1}+E0) \cdot (E3+E2+\overline{E1}+\overline{E0})$$

$$P0(E3,E2,E1,E0) = (E3+E2+E1+E0) \cdot (E3+E2+E1+\overline{E0}) \cdot (E3+\overline{E2}+E1+E0) \cdot (E3+\overline{E2}+E1+\overline{E0}) \cdot (E3+\overline{E2}+\overline{E1}+E0) \cdot (E3+\overline{E2}+\overline{E1}+\overline{E0})$$

$$V(E3,E2,E1,E0) = (E3+E2+E1+E0)$$

Step 4 : Karnaugh Map (0.75 point)

E3E2 \ E1E0	00	01	11	10
00	0	1	1	1
01	0	1	1	1
11	0	1	1	1
10	0	1	1	1


E3E2 \ E1E0	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	1	0	1	1
10	1	0	1	1

$$P1(E3,E2,E1,E0) = E3+E2$$

$$P0(E3,E2,E1,E0) = (E3+E1) \cdot (E3+\overline{E2})$$

$$V(E3,E2,E1,E0) = E3+E2+E1+E0 \text{ (no more simplification possible)}$$

Step 5 : Schematics (1 point)

 


2. The input 0000 produces the output $(P1, P0) = (0,0)$ and $V = 0$. (0.5 point)

and the input 0001 produces the output $(P1,P0) = (0,0)$ and $V = 1$. (0.5 point)

That explains the V output purpose. It allows the differentiation between the absence of priority and the priority with level 0. (1 point)

Exercise 3 : (4 points)

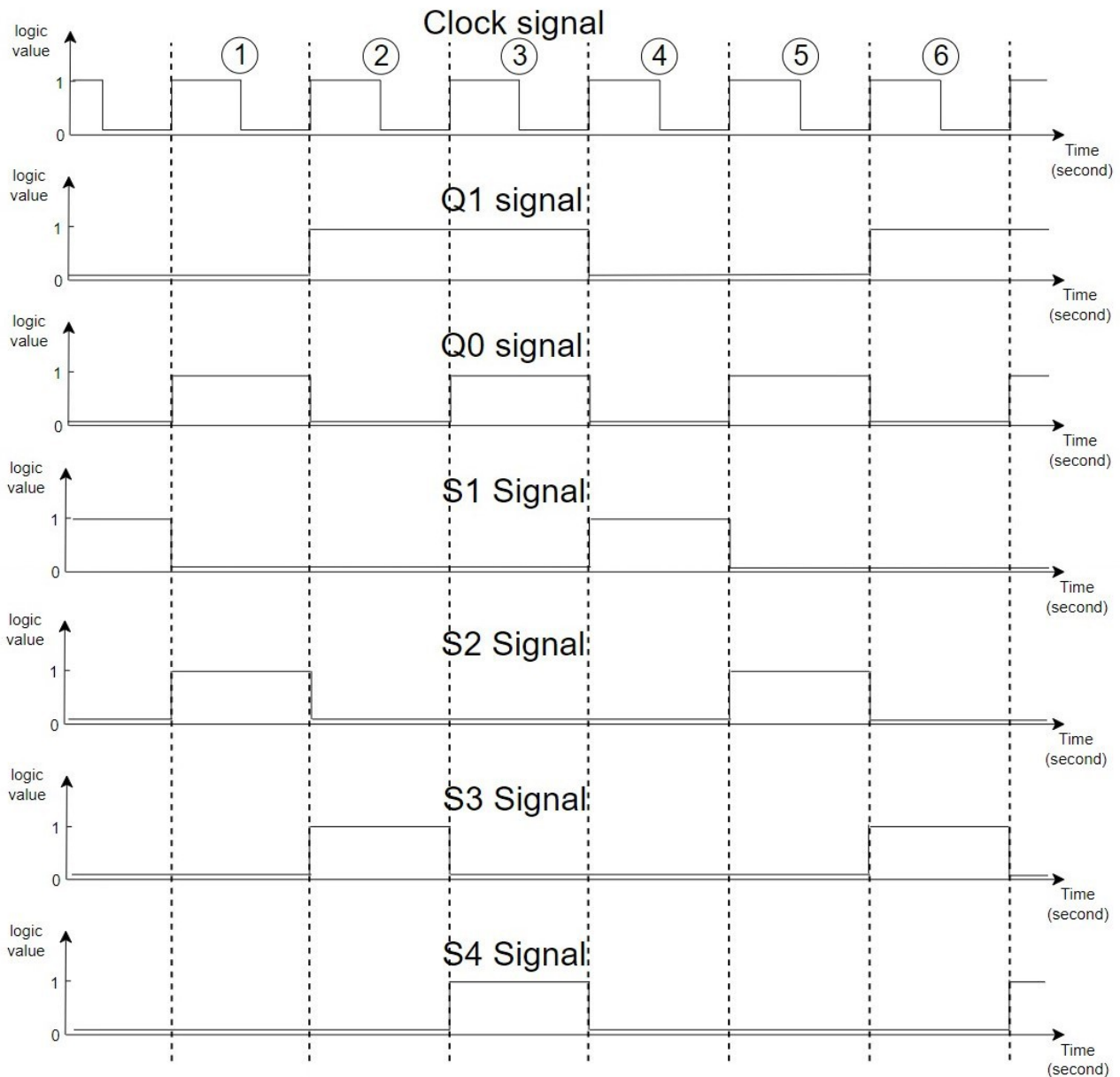
1. The timing diagram of the circuit : (0.5 point for each cycle)




2. The 2 FlipFlops implement a 2 bits Counter. (1 point)

Exercise 4 : (7 points)

Step 1 : Global Scheme (1 point)

 

Step 2 : F.S.M. (1 point)

 

Note : The cases where L and R are not pressed, or they are pressed together at the same time, are not presented in the diagram for simplicity.

Step 3 : Transition Table (1 point)

Current State	L	R	Next State
S0	0	0	S0
S0	0	1	S1
S0	1	0	S3
S0	1	1	S0

S1	0	0	S1
S1	0	1	S2
S1	1	0	S0
S1	1	1	S1
S2	0	0	S2
S2	0	1	S3
S2	1	0	S1
S2	1	1	S2
S3	0	0	S3
S3	0	1	S0
S3	1	0	S2
S3	1	1	S3

Step 4 : Encoded States Table and Outputs Table (1 point)

State	S ₁	S ₀	N	E	S	W
S0	0	0	1	0	0	0
S1	0	1	0	1	0	0
S2	1	0	0	0	1	0
S3	1	1	0	0	0	1

Step 5 : Encoded Transition Table (1 point)

S ₁	S ₀	L	R	S' ₁	S' ₀
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	1
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	0	1
1	0	0	0	1	0
1	0	0	1	1	1
1	0	1	0	0	1
1	0	1	1	1	0

1	1	0	0	1	1
1	1	0	1	0	0
1	1	1	0	1	0
1	1	1	1	1	1

Step 6 : Logical Functions (1 point)

$$N(S_1, S_0) = \bar{S}_1 \cdot \bar{S}_0$$

$$E(S_1, S_0) = \bar{S}_1 \cdot S_0$$

$$S(S_1, S_0) = S_1 \cdot \bar{S}_0$$

$$W(S_1, S_0) = S_1 \cdot S_0$$

$\begin{array}{c} \text{LR} \\ \hline S_1 S_0 \end{array}$	00	01	11	10
00	0	0	1	1
01	0	1	0	1
11	0	0	1	1
10	1	0	1	0

$\begin{array}{c} \text{LR} \\ \hline S_1 S_0 \end{array}$	00	01	11	10
00	0	1	1	0
01	1	0	0	1
11	0	1	1	0
10	1	0	0	1

$$S'_1(S_1, S_0, L, R) = \bar{S}_1 \cdot S_0 \cdot \bar{L} \cdot R + \bar{S}_1 \cdot \bar{S}_0 \cdot L \cdot \bar{R} + S_1 \cdot \bar{L} \cdot \bar{R} + S_1 \cdot \bar{S}_0 \cdot R + S_1 \cdot S_0 \cdot L$$

$$S'_0(S_1, S_0, L, R) = S_0 \cdot \bar{L} \cdot \bar{R} + S_0 \cdot L \cdot R + \bar{S}_0 \cdot L \cdot \bar{R} + \bar{S}_0 \cdot \bar{L} \cdot R$$

Step 7 : Schematics (1 point)

