

Machine Structures 2 resit exam solution

Exercise 1 : (4 points)

1. In Digital Electronics, information is fundamentally represented using the binary system, (relies only two distinct values 1 and 0, also considered correct). (1 point)

2. The Boolean expression for an XOR gate with inputs A and B and output S is :

$$S = A \oplus B \text{ (0.5 point)}$$

Truth Table of an XOR gate : (0.5 point)

A	B	S
0	0	0
0	1	1
1	0	1
1	1	0

3. A D-Latch is transparent when the clock is at 1. (0.5 point)

And The D-FlipFlop is transparent while the rising edge (or passing from 0 to 1) of the clock. (0.5 point)

4. The values inside the FlipFlops register of a Sequential Circuit represent the encoding States of the F.S.M related to the Sequential Circuit. (1 point)

Exercise 2 : (5 points)

5-step method to design the Decoder 4-2 :

Step 2 : Truth Table (1 point)

E1	E0	S0	S1	S2	S3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Step 3 : Canonical Disjunctive Functions (1 point)

$$S_0(E_1, E_0) = \overline{E_1} \cdot \overline{E_0}$$

$$S_1(E_1, E_0) = \overline{E_1} \cdot E_0$$


$$S_2(E_1, E_0) = E_1 \cdot \overline{E_0}$$

$$S_3(E_1, E_0) = E_1 \cdot E_0$$

Step 4 : Karnaugh Map

No more simplification is possible.

Step 5 : Schematics (1 point)

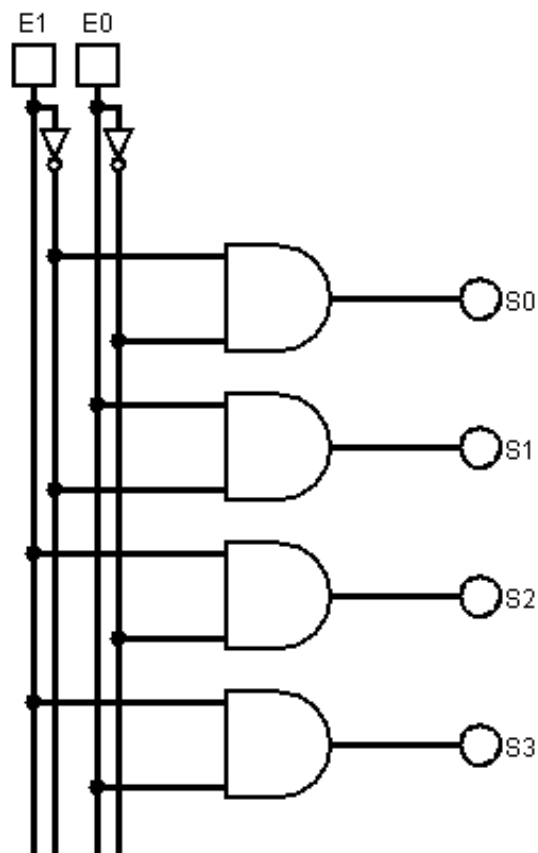


1. Inputs : $(E_1, E_0) = (0, 0)$ and $(I_n, I_2, I_1, I_0) = (0, 0, 0, 1)$, the circuit *output* = 1 (0.5 point)

Inputs : $(E_1, E_0) = (1, 1)$ and $(I_n, I_2, I_1, I_0) = (1, 1, 1, 1)$, the circuit *output* = 1 (0.5 point)

2. The circuit created in the schematics is a : Multiplexer 4-1 (1 point)

Exercise 3 : (4 points + 1 point)

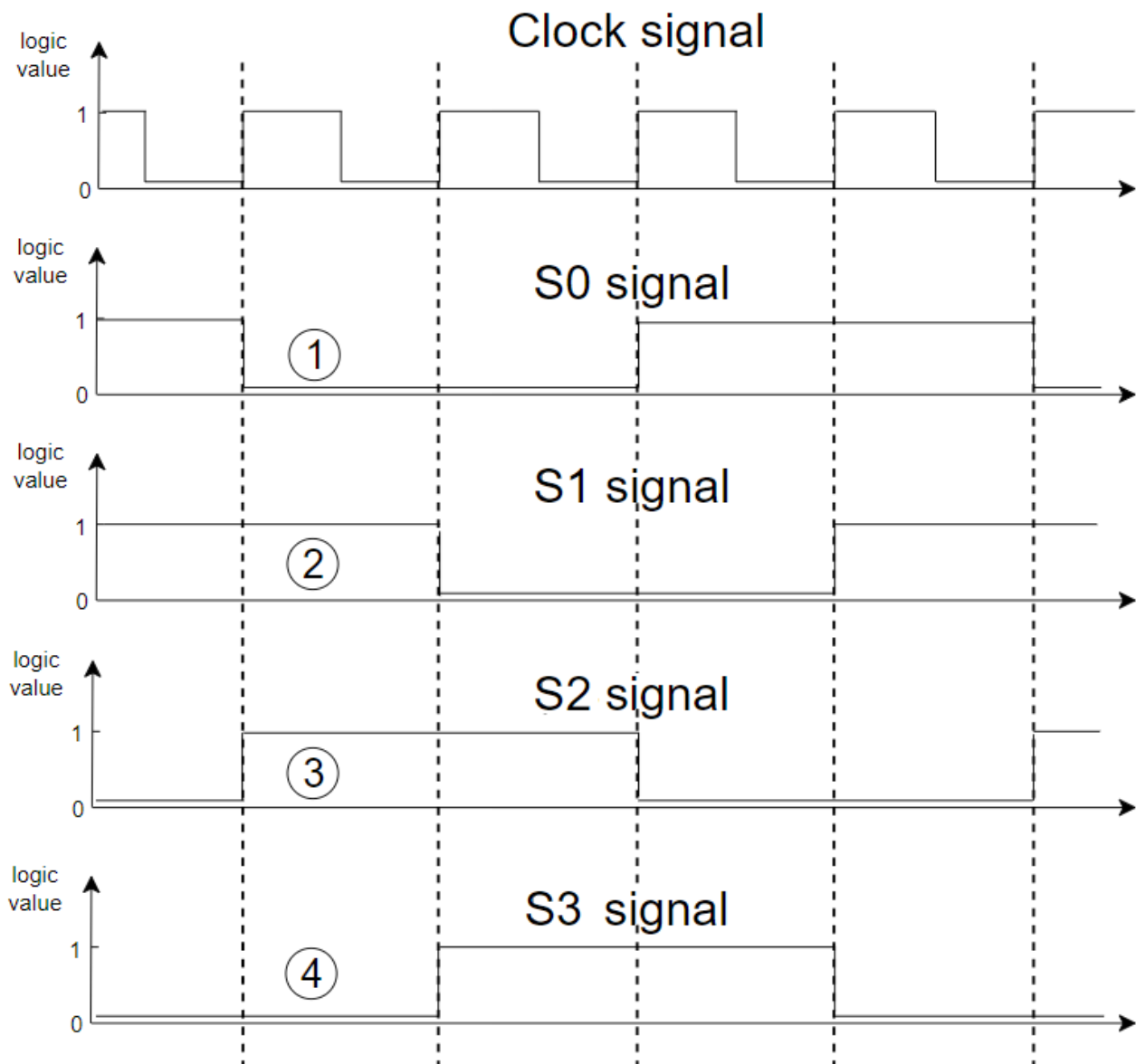
1. The timing diagram of the circuit : (1 point for each signal)



2. Name the circuit is : Circular SIPO Shifter. (same meaning as Circular is accepted)
(1 point)


Exercise 4 : (7 points)

Step 1 : Global Scheme (1 point)

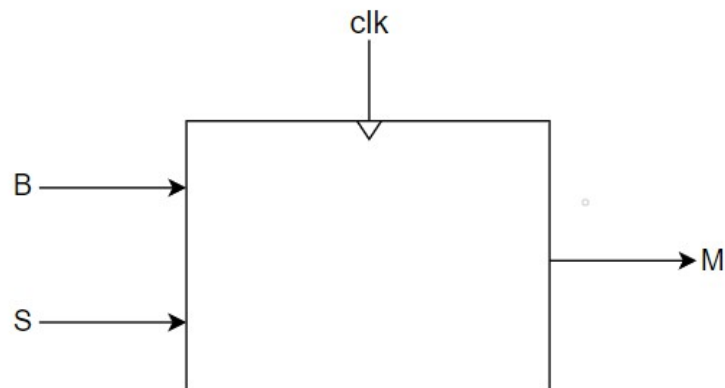

B : Button
S : Sensor
M : Motor

Step 2 : F.S.M. (1 point)

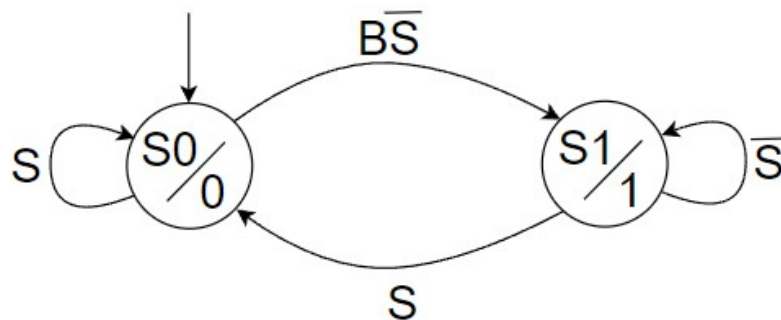

Note : Only the most important transitions are depicted in the F.S.M.

Step 3 : Transition Table (1 point)

Current State	B	S	Next State
S0	0	0	S0
S0	0	1	S0
S0	1	0	S1
S0	1	1	S0
S1	0	0	S1
S1	0	1	S0
S1	1	0	S1
S1	1	1	S0

Step 4 : Encoded States Table and Outputs Table (1 point)

State	S_t	M
S0	0	0
S1	1	1

Note : We name the state encoding S_t to make it different from S, the sensor input.

Step 5 : Encoded Transition Table (1 point)

S_t	B	S	S_t'
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Step 6 : Logical Functions (1 point)

$M(S_t) = S_t$ (directly extracted)

$S_t \backslash B \ S$	00	01	11	10
0	0	0	0	1
1	1	0	0	1

$$S_t'(S_t, B, S) = B \cdot \bar{S} + S_t \cdot \bar{S}$$

Step 7 : Schematics (1 point)

